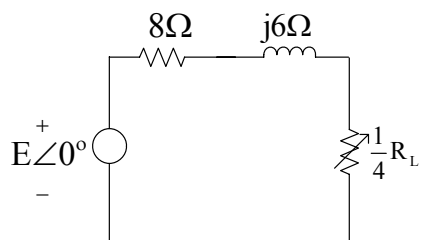


## 第六篇 最大功率傳輸 練習題解答

1. (A) 將阻抗歸至一次側可得下圖



當  $\frac{1}{4}R_L = |8 + j6|$  時可得最大功率傳輸

$$\frac{1}{4}R_L = \sqrt{8^2 + 6^2} = 10$$


$$R_L = 40$$

2. (D) 將負載端開路，可得看入之等效阻抗  $Z_{Th}$

$$Z_{Th} = 1 // j = \frac{1}{2} + j\frac{1}{2}$$

當  $Z_L = Z_{Th}^* = \frac{1}{2} - j\frac{1}{2}$  可得最大功率傳輸

3. (B) 原電路可得下圖等效電路

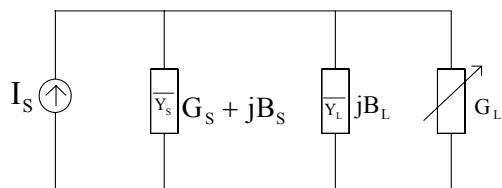

因  $B_L$  固定，可視為已知歸至  $Y_s$  處，則  $G_L$  依最大功率傳輸定理，可得

$$\begin{aligned} G_L &= |G_s + j(B_s + B_L)| \\ &= \sqrt{G_s^2 + (B_s + B_L)^2} \end{aligned}$$

4. (D) 因  $\theta_L = 60^\circ$  為固定值，由最大功率傳輸定理知，當  $|Y_L| = |Y_s|$  時可得最大功率傳輸，即


$$|Y_L| = |Y_s| = \sqrt{G_s^2 + B_s^2}$$

$$Y_L = |Y_L| \angle 60^\circ = |Y_L| \cos 60^\circ + j |Y_L| \sin 60^\circ = G_L + jB_L$$

$$G_L = |Y_L| \cos 60^\circ = \frac{1}{2} |Y_L|$$

$$G_L = \frac{1}{2} \sqrt{G_s^2 + B_s^2}$$

5. (A)

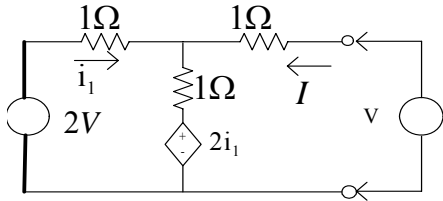

由網目分析

$$\begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ I \end{bmatrix} = \begin{bmatrix} 2 - 2i_1 \\ V - 2i_1 \end{bmatrix}, \quad \begin{bmatrix} 4 & 1 \\ 3 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ I \end{bmatrix} = \begin{bmatrix} 2 \\ V \end{bmatrix}$$

$$I = \begin{bmatrix} 4 & 2 \\ 3 & V \\ 4 & 1 \\ 3 & 2 \end{bmatrix} = \frac{4}{5}V - \frac{6}{5}, \quad V = \frac{5}{4}I + \frac{3}{2}$$

$$R_{Th} = \frac{5}{4} \Omega = R_{ab}, \quad V_{Th} = \frac{3}{2} V$$

6. (D)

由最大功率傳輸定理知，當  $R_L = R_{in} = \frac{5}{4}$  可得  $P_{max}$

$$P_{max} = \left[ \frac{\frac{3}{2}}{\frac{5}{4} + \frac{5}{4}} \right]^2 \times \frac{5}{4} = 0.45(W)$$

7. (C)


當  $R_L = |Z| = \sqrt{40^2 + 30^2} = 50 \Omega$  時，可得最大功率傳輸。

8. (C)

欲得最大功率傳輸，負載  $Z_L = Z_{Th}^* = 8 - j4 \Omega$

$$P_{max} = \left( \frac{160}{8+8} \right)^2 \times 8 = 800 (W)$$

9. (B)

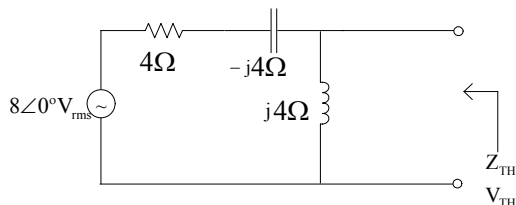

$$Z_{Th} = j4 // (4 - j4) = 4 + j4$$

$$Z_L = Z_{Th}^* = 4 - j4 \Omega$$

$$V_{Th} = \frac{j4}{4 - j4 + j4} \times 8 = 8 \angle 90^\circ$$

10. (C)

$$P_{\max} = \left(\frac{8}{4+4}\right)^2 \times 4 = 4 \text{ (W)}$$