


第一篇 阻抗轉換 練習題解答

1. (D)

$$Z_A = 5 \times 10 \times \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{j5} \right) = 50 \times \frac{10 + j15}{j50} = 15 - j10$$


2. (B)

圖(b)經 $\Delta \rightarrow Y$ 互換可得

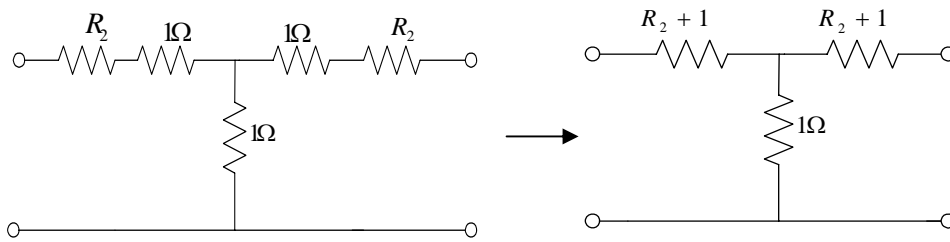

與圖(a)比較可得 $R_1 = 1\Omega$, $R_2 = 2\Omega$

3. (A)

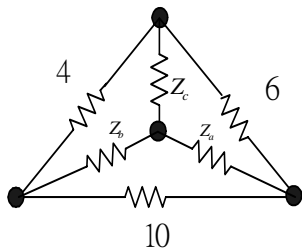


$$Z_a = \frac{6 \times 10}{4 + 6 + 10} = 3\Omega$$

$$Z_b = \frac{4 \times 10}{4 + 6 + 10} = 2\Omega$$

$$Z_c = \frac{4 \times 6}{4 + 6 + 10} = 1.2\Omega$$

4. (A)

$\Delta - Y$ 互換

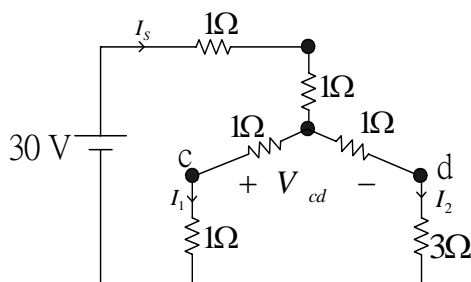

$$R_{ab} = [(1+1) // (1+3)] + 2 = 3\frac{1}{3}\Omega$$

5. (B)


$$I_s = \frac{30}{R_{ab}} = 9(A)$$

$$\begin{cases} I_1 = \frac{4}{2+4} \times 9 = 6 & \Rightarrow V_c = 1 \times I_1 = 6(V) \\ I_2 = \frac{2}{2+4} \times 9 = 3 & \Rightarrow V_d = 3 \times I_1 = 9(V) \end{cases}$$

$$V_{cd} = V_c - V_d = -3(V)$$

分
流
處
理

6. (D)

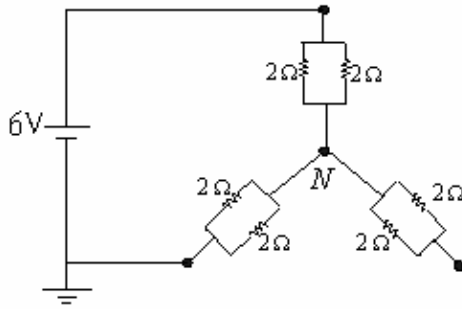

$$V_N = \frac{1}{1+1} \times 6 = 3V$$

7. (D) $Z_1 = 10K$, $Z_2 = j\omega L$, $Z_3 = 5K$, $Z_4 = \frac{1}{j\omega C}$

電橋平衡 $Z_1 Z_4 = Z_2 Z_3$, $C = \frac{L}{5K \times 10K} = 20pF$

8. (C)

9. (A)

$$1K \times 5.6K = 1.6K \times 3.5K$$

電橋平衡 $I_G = 0$

10. (A)

電橋平衡：

$$R \times j5 = 3 \times j3 \quad \rightarrow \quad R = \frac{9}{5} \Omega$$